

# Operational Transconductance Amplifier

EDC2 project

Catana Dominic Costin

1231EB


# Content

1. Problem.....	2
2. DC Circuit.....	3
3. LTSpice simulation.....	4
4. Finding the best $V_g$ .....	6

# 1. Problem

A two-stage Operational Transconductance Amplifier (OTA) with a differential input and a single-ended output, implemented using bipolar transistors, is shown below.

 
1. Calculate the theoretical expressions of the DC collector currents of bipolar transistors Q1 - Q8, considering  $V_{BE} \approx 0.6V$ . Calculate the theoretical expression of the small-signal voltage gain  $A_V = V_O/V_g$ .
2. Implement the schematic in a circuit simulation software (LTSpice). Design the circuit (i.e. select transistor types for Q1 - Q8, choose a value for  $R_2$  and  $C_{inf}$  in order to have a (theoretical) gain value  $A_V = 1250$ .
3. Simulate the circuit (transient, AC sweep), choosing an appropriate amplitude for  $V_g$  in order to minimize output signal distortion.
4. Compare the theoretical  $A_V$  value from point b) with the value obtained from the simulation. Name a possible cause for differences between the two values.
5. Specify a method for decreasing the voltage gain (without changing  $R_1$ ,  $R_2$ ,  $V_{CC}$  or  $V_{CM}$ ). Implement the change and re-simulate the circuit in order to demonstrate the effect.


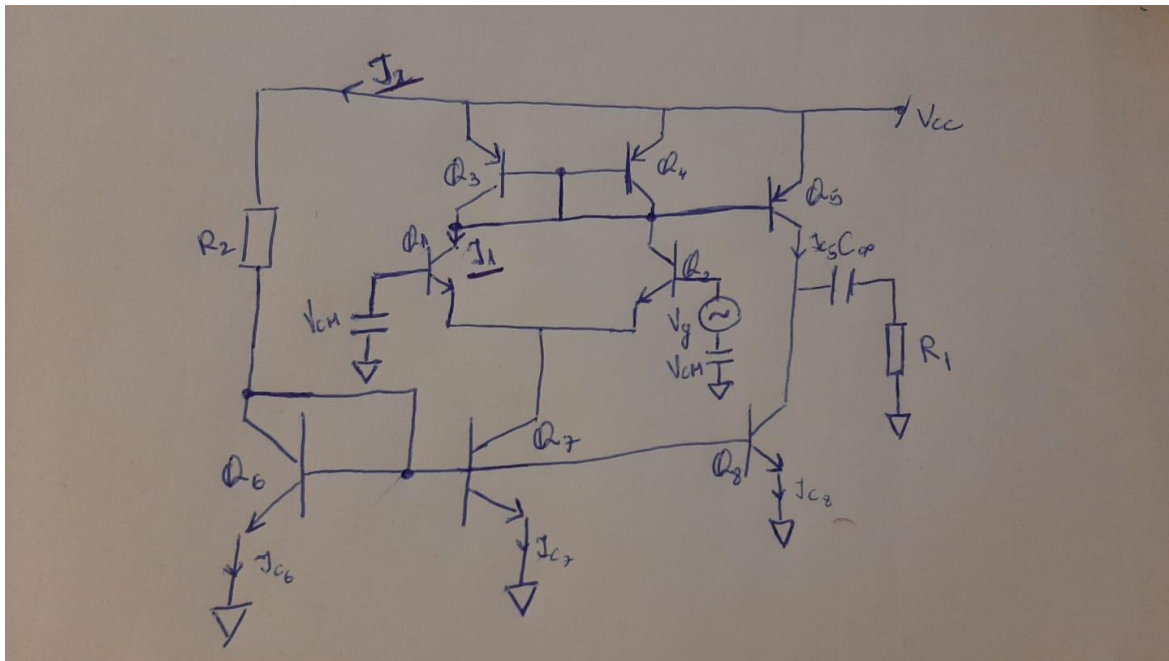
## 2. DC Circuit

We have the represented scheme in the problem with the intensities  $I_1$  and  $I_2$  taking in consideration that  $I_2$  passes through  $R_2$  and  $I_1$  through  $Q_1$ .  $Q_6$ ,  $Q_7$  and  $Q_8$  being current mirrors with  $Q_3$  and  $Q_4$ , the current is passing and is exiting with the same intensity( $I_2$ ).

$Q_6$  – input terminal for the transistors on the bottom. ( $Q_6$ ,  $Q_7$  and  $Q_8$ )



This means that the currents  $I_1$  and  $I_2$  are equal with the same values with the intensities that correspond with the transistors:

$$I_1 = I_{C1} + I_{C2} + I_{C3} + I_{C4}$$

$$I_2 = I_{C5} + I_{C6} + I_{C7} + I_{C8}$$

$$V_{BE} = V_{CE} = 0.6V$$

Writing for the branch from  $V_{CC}$  from  $Q_6$  we have then:

$$V_{CC} = R_2 I_2 + V_{CE} \Rightarrow I_2 = (V_{CC} - V_{CE})/R_2$$

Writing for the branch from  $V_{CC}$  from  $Q_7$  we have then:

$$I_1 = (V_{CC} - V_{CE})/2 \cdot R_2$$

### 3. LTSpice simulation


We used at the implementation of the circuit:

NPN transistors: BC847B at Q<sub>1</sub>, Q<sub>2</sub>, Q<sub>6</sub>, Q<sub>7</sub>, Q<sub>8</sub>

PNP transistors: BC857B at Q<sub>3</sub>, Q<sub>4</sub>, Q<sub>5</sub>


$$C_{inf} = 1F$$
$$V_{CM} = 1.5V$$
$$V_{CC} = 10V$$
$$R_1 = 313k$$
$$R_2 = 10k$$

The scheme of the circuit in LTSpice:

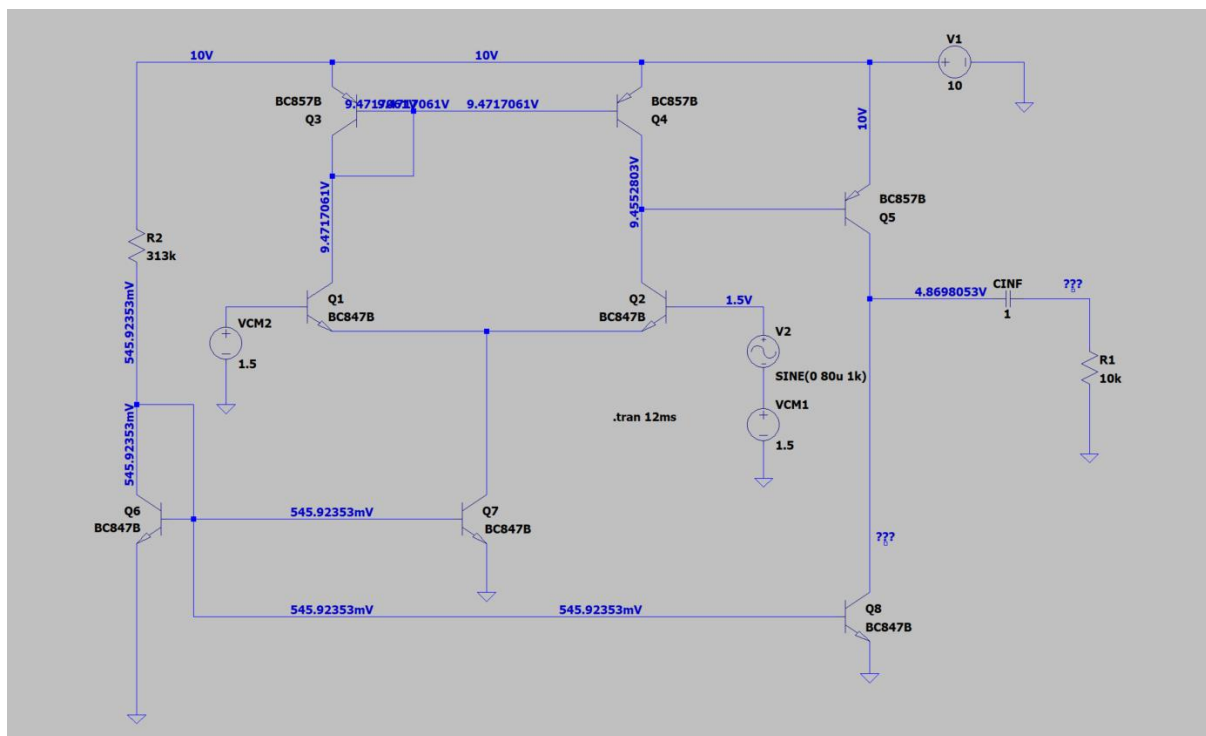


# Operational Transconductance Amplifier


Intensities at  $Q_1$ :

 


At  $Q_1$  and  $Q_6$ :

 


At  $R_1$ :

 

At  $R_2$ :

 

At  $Q_7$ :

 

## 4. Finding the best $V_g$

On transient simulation:

